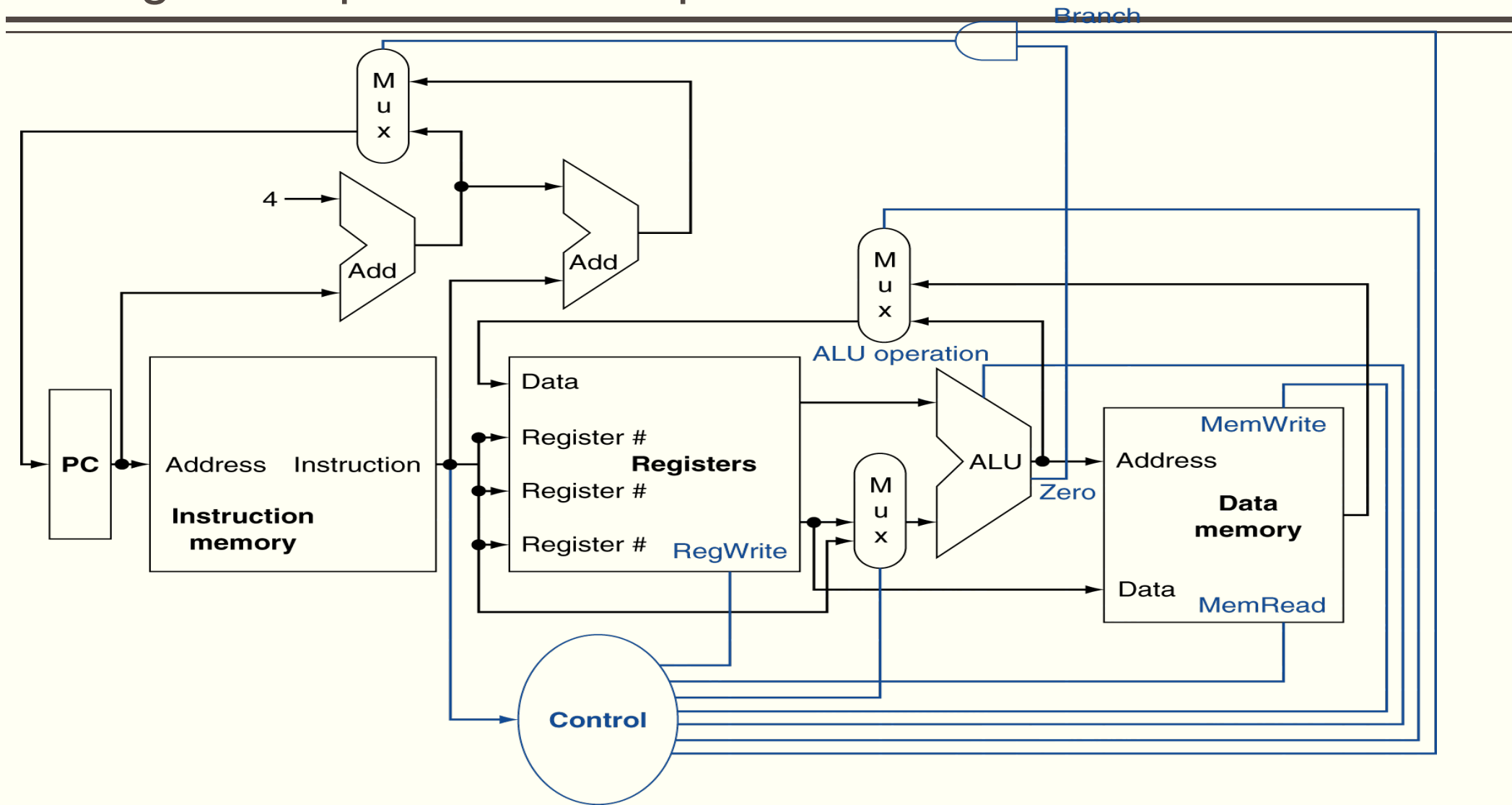



Verilog Description of MIPS processor



Multiplexer

```
module Mult2to1(In1,In2,Sel,Out);  
  input [31:0] In1,In2;  
  input Sel;  
  output reg [31:0] Out;  
  always @(In1,In2,Sel)  
  case (Sel)  
    0: Out <=In1;  
    default: Out <=In2;  
  endcase  
endmodule
```


MIPS ALU

 

MIPS ALU

```
module MPISALU(ALUctl,A,B,ALUOut,Ze);
  input [3:0] ALUctl;
  input [31:0] A,B;
  output reg [32:0] ALUOut;
  output Ze;
  assign Ze = (ALUOut == 0);
  always@(ALUctl,A,B) begin
    case (ALUctl)
      0: ALUOut <= A & B;
      1: ALUOut <= A | B;
      2: ALUOut <= A + B;
      6: ALUOut <= A - B;
      7: ALUOut <= A < B ? 1 : 0;
      12 : ALUOut <= ~(A|B);
      default : ALUOut <= 0;
    endcase
  end
endmodule
```

MIPS Register File Verilog Description

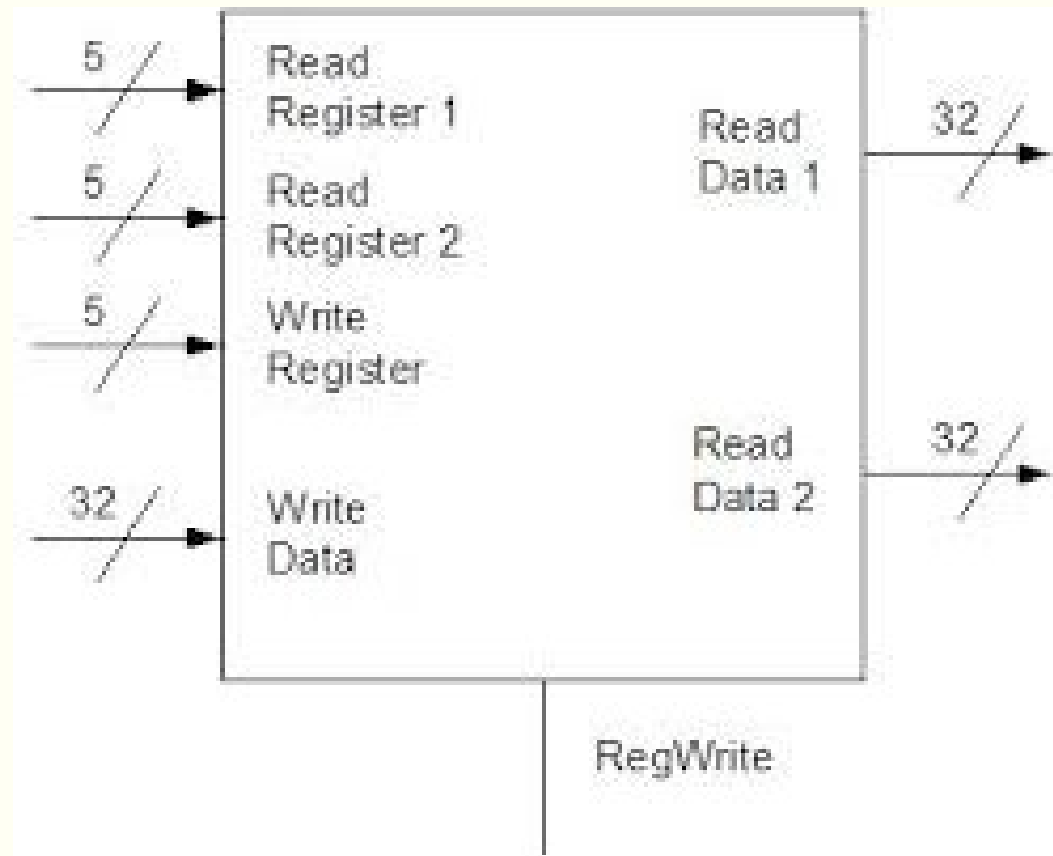

MIPS Register file

```
module registerfile(Read1,Read2,WriteReg,  
    WriteData, RegWrite, Data1,Data2,Clock);  
  
    input [4:0] Read1,Read2,WriteReg;  
    input [31:0] WriteData;  
    input RegWrite, Clock;  
  
    output[31:0] Data1, Data2;  
    reg[ 31:0] RF [31:0];  
  
    assign Data1 = RF[Read1];  
    assign Data2 = RF[Read2];  
  
    always @(posedge Clock)  
        if (RegWrite) RF[WriteReg] = WriteData;  
endmodule
```

MIPS Instruction Format

(Register) Format:

Opcode (6)	Rs (5)	Rt (5)	Rd (5)	Shamt (5)	Function (6)
---------------	-----------	-----------	-----------	--------------	-----------------

add \$1, \$2, \$3

0000000001000110000100000100000

Instruction Fetch

```
module CPU (clock);
    input clock;
    reg[31:0] PC, Regs[0:31], IMemory[0:1023], DMemory[0:1023], IR,ALUOut;
    wire [4:0] rs, rt;
    wire [31:0] Ain, Bin;
    wire [5:0] op;
    assign rs = IR[25:21];
    assign rt = IR[20:16];
    assign op = IR[31:26];
    initial begin
        PC = 0;
    end
    always @ (posedge clock)
    begin
        IR <= IMemory[PC>>2];
        PC <= PC + 4;
    end
endmodule
```


ADD Instruction

```
always @ (posedge clock)
begin
    IR <= IMemory[PC>>2];
    PC <= PC + 4;
    if (op == 6'b000000)
        case (IR[5:0])

            32 : ALUOut <= Ain + Bin;

        endcase
    end
endmodule
```